

國立高雄科技大學
電子工程系(第一校區)

硬體描述語言

Lab 3

指導教授：陳銘志

班 級：電子三甲

學生姓名：蕭詠釗

學 號：C111112132

Lab 3.

1. A *full subtractor* has three 1-bit inputs x , y , and z (previous borrow) and two 1-bit outputs D (difference) and B (borrow).

The logic equations for D and B are as follows:

$$D = x'y'z + x'yz' + xy'z' + xyz$$

$$B = x'y + x'z + yz$$

Write the full Verilog description (**dataflow modeling**) for the full subtractor module, including I/O ports (Remember that $+$ in logic equations corresponds to a logical or operator ($||$) in dataflow). Instantiate the subtractor inside a stimulus block and test all eight possible combinations of x , y , and z given in the following truth table. (Hint: Each test pattern has a delay of 10 ns, and the simulation is finished at 200 ns.)

x	y	z	B	D
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	1	0
1	0	0	0	1
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

主(電路)程式

```
'timescale 1ns / 1ps

module lab4(D, B, x, y, z);
output D, B;
input x, y, z;
wire D, B;
assign D=((~x)&(~y)&z)|((~x)&y&(~z))|(x&(~y)&(~z))|(x&y&z);
assign B= ((~x)&y)|((~x)&z)|(y&z);
endmodule
```


測試程式(testbench)

```
'timescale 1ns / 1ps
module lab4tb();
reg x, y, z;
wire D, B;


// Instantiate the 4-bit full adder. call it FA1_4
lab4 UU1(D, B, x, y, z);
initial
begin

$monitor($time, " x= %b, y=%b, z= %b, --- D= %b, B= %b\n",
x, y, z, D, B);
end
// Stimulate inputs
initial
begin
x = 1'b0 ; y =1'b0; z=1'b0;
#10 x = 1'b0 ; y =1'b0; z=1'b1;
#10 x = 1'b0 ; y =1'b1; z=1'b0;
#10 x = 1'b0 ; y =1'b1; z=1'b1;
#10 x = 1'b1 ; y =1'b0; z=1'b0;
#10 x = 1'b1 ; y =1'b0; z=1'b1;
#10 x = 1'b1 ; y =1'b1; z=1'b0;
#10 x = 1'b1 ; y =1'b1; z=1'b1;
end
initial #200 $finish;


endmodule
```

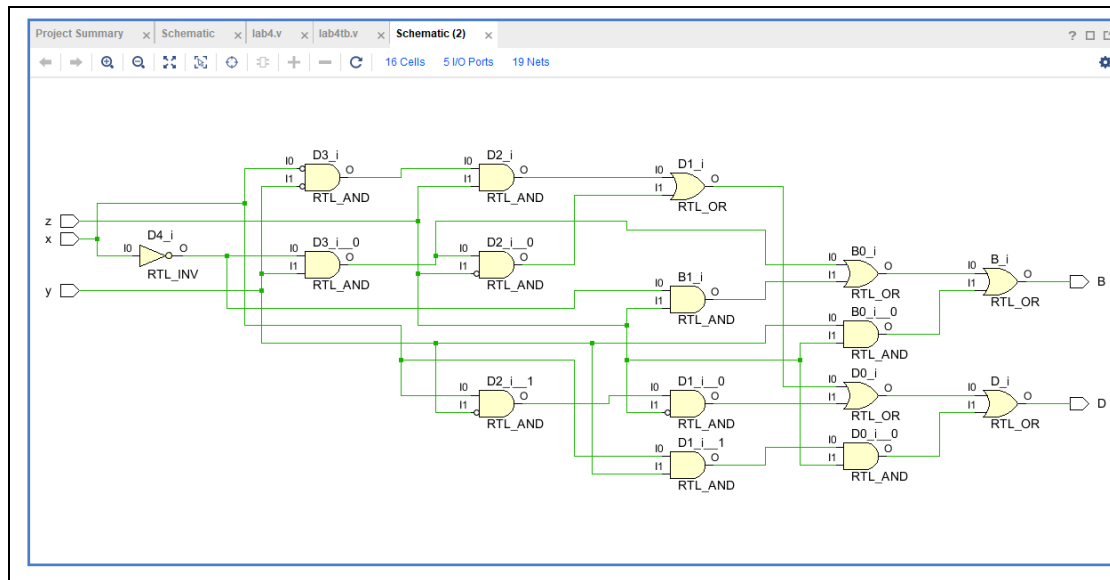



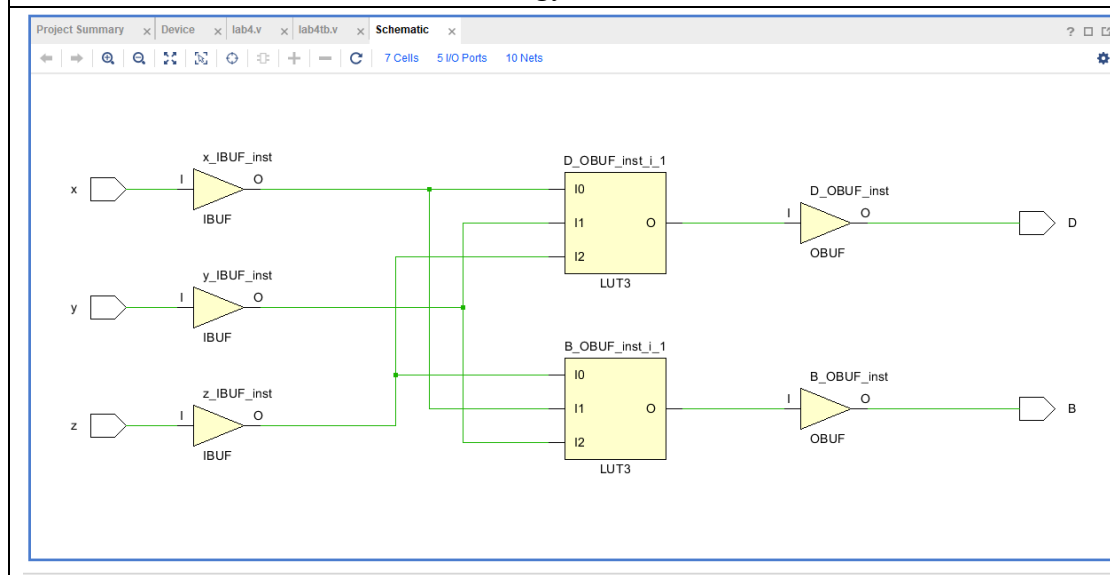

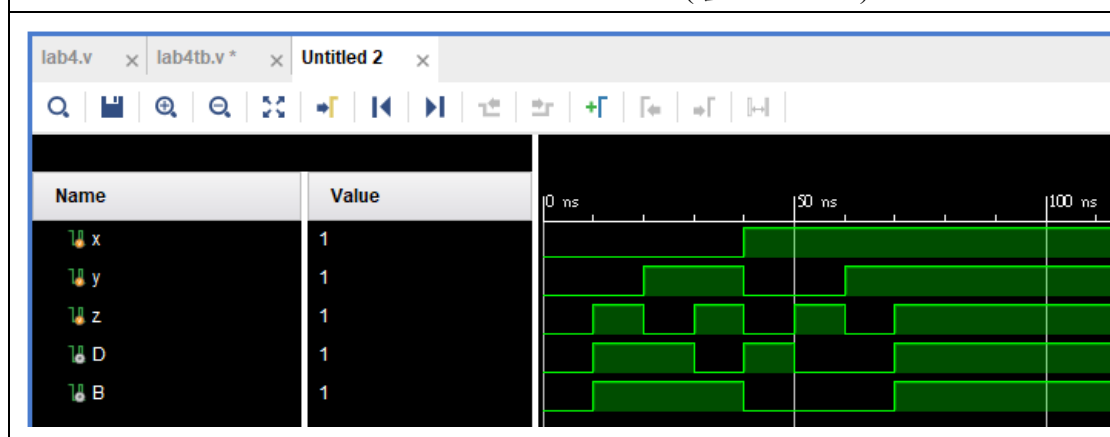


Technology Schematic



Behavioral Simulation Waveform(含 \$monitor)



Tcl Console x Messages Log



```
# run 1000ns  
0 x= 0, y=0, z= 0, --- D= 0, B= 0  
  
10 x= 0, y=0, z= 1, --- D= 1, B= 1  
  
20 x= 0, y=1, z= 0, --- D= 1, B= 1  
  
30 x= 0, y=1, z= 1, --- D= 0, B= 1  
  
40 x= 1, y=0, z= 0, --- D= 1, B= 0  
  
50 x= 1, y=0, z= 1, --- D= 0, B= 0  
  
60 x= 1, y=1, z= 0, --- D= 0, B= 0  
  
70 x= 1, y=1, z= 1, --- D= 1, B= 1  
  
$finish called at time : 200 ns : File "C:/Users/User/project_1/project_1.srscs/sim_1/new/lab4tb.v" Line 31
```

-----作答區結束-----

- 2.** If the equations D, B have regular delays of 「 10 」 and 「 20 」 ns respectively, please use the same truth table as above to simulate the operation results. Please show the correct results of D, and B after the simulation. (Hint: Each test pattern has a delay of 10 ns, and the simulation is finished at 200 ns.)

主(電路)程式

```
'timescale 1ns / 1ps

module lab4(D, B, x, y, z);
output D, B;
input x, y, z;
wire D, B;
assign D = ((~x)&(~y)&z) | ((~x)&y&(~z)) | (x&(~y)&(~z)) | (x&y&z);
assign B = ((~x)&y) | ((~x)&z) | (y&z);
endmodule
```


測試程式(testbench)

```
'timescale 1ns / 1ps
module lab4tb();
reg x, y, z;
wire #10 D;
wire #20 B;


lab4 UU1(D, B, x, y, z);
initial
begin

$monitor($time, " x= %b, y=%b, z= %b, --- D= %b, B= %b\n",
x, y, z, D, B);
end
// Stimulate inputs
initial
begin
x = 1'b0 ; y =1'b0; z=1'b0;
#10 x = 1'b0 ; y =1'b0; z=1'b1;
#10 x = 1'b0 ; y =1'b1; z=1'b0;
#10 x = 1'b0 ; y =1'b1; z=1'b1;
#10 x = 1'b1 ; y =1'b0; z=1'b0;
#10 x = 1'b1 ; y =1'b0; z=1'b1;
#10 x = 1'b1 ; y =1'b1; z=1'b0;
#10 x = 1'b1 ; y =1'b1; z=1'b1;
end
initial #200 $finish;


endmodule
```

 

Technology Schematic

 

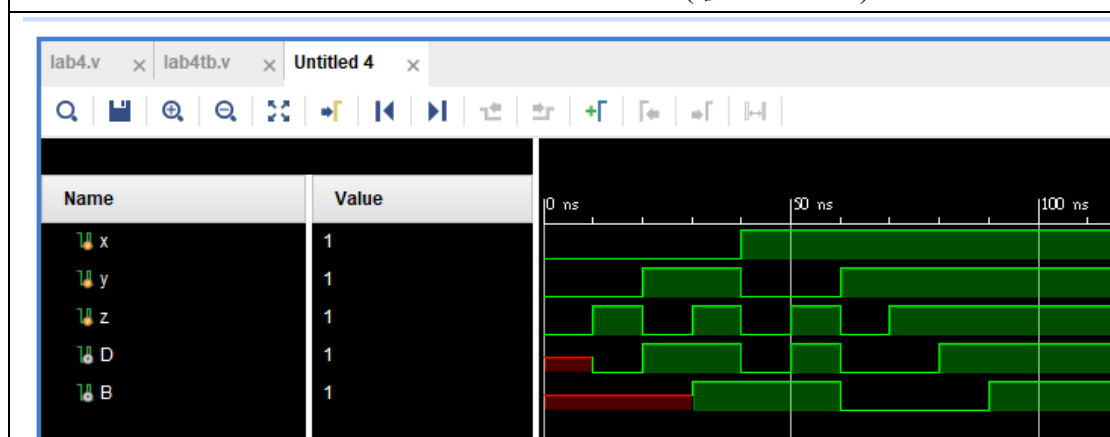Behavioral Simulation Waveform(含 \$monitor)




```
Tcl Console x Messages Log
[Icons: Search, Zoom In, Zoom Out, Run, Copy, Paste, Delete]

# }
# }
# run 1000ns
    0 x= 0, y=0, z= 0, --- D= x, B= x
    10 x= 0, y=0, z= 1, --- D= 0, B= x
    20 x= 0, y=1, z= 0, --- D= 1, B= x
    30 x= 0, y=1, z= 1, --- D= 1, B= 1
    40 x= 1, y=0, z= 0, --- D= 0, B= 1
    50 x= 1, y=0, z= 1, --- D= 1, B= 1
    60 x= 1, y=1, z= 0, --- D= 0, B= 0
    70 x= 1, y=1, z= 1, --- D= 0, B= 0
    80 x= 1, y=1, z= 1, --- D= 1, B= 0
    90 x= 1, y=1, z= 1, --- D= 1, B= 1

$finish called at time : 200 ns : File "C:/Users/User/project_1/project_1.srscs/sim_1/new/lab4tb.v" Line 31
INFO: [USF-XSim-96] XSim completed. Design snapshot 'lab4tb_behav' loaded.
INFO: [USF-XSim-97] XSim simulation ran for 1000ns
```

-----作答區結束-----