

國立高雄科技大學
電子工程系(第一校區)

硬體描述語言

Lab. 8: Finite State Machine

指導教授：陳銘志

班 級：電子三甲

學生姓名：蕭詠釗

學 號：C111112132

Lab. 8: Finite State Machine

1. Please use Verilog HDL to implement the Mealy Finite State Machine in Figure 1 .

- Clock period is 20ns.
- All states must be passed, the order is $S0 \rightarrow S1 \rightarrow S2 \rightarrow S3 \rightarrow S4 \rightarrow S0 \rightarrow S1$.
- The unstable state of the output signal cannot exceed half of the period.
- The signals to be included in \$monitor are the following three, **in**, **State** and **out**.
- Total simulation time is 150ns


 


Figure 1 Mealy FSM

作業目標

- 透過調整測試程式使狀態機正常的改變狀態。
 - 狀態機運行流程：S0→S1→S2→S3→S4→S0→S1.
 - 狀態改變的間隔時間：10 ns
 - Total Simulation Time：150ns

作業範例

 

片段測試程式

```

initial begin
    #20 reset = 1;
    #20 reset = 0;
    #15 in = 1 ;
    #30 in = 0 ;
    #15 in = 1 ;
    #15 in = 0 ;
end

initial begin
    #150 $finish;
end
    
```

作業作答格式

檢附項目：主(電路)程式、測試程式、RTL schematic、Technology Schematic、Behavioral Simulation Waveform(含 \$monitor)，(每一項 18 分)。

-----第一題作答區-----

主(電路)程式

```

module count (
    input clk,
    input reset,
    input in,
    output reg out,
    
```

```

output reg [2:0] currentstate,
output reg [2:0] nextstate
);
parameter [2:0] s0 = 3'd0,
                s1 = 3'd1,
                s2 = 3'd2,
                s3 = 3'd3,
                s4 = 3'd4;
always @(posedge clk) begin
    if (reset)
        currentstate <= s0;
    else
        currentstate <= nextstate;
end
always @(currentstate or in) begin
    case(currentstate)
        s0: begin
            if (in) begin
                nextstate <= s1;
                out <= 1'd1;
            end else begin
                nextstate <= s0;
                out <= 1'd0;
            end
        end
        s1: begin
            if (in) begin
                nextstate <= s2;
                out <= 1'd0;
            end else begin
                nextstate <= s1;
                out <= 1'd1;
            end
        end
        s2: begin
            if (in) begin
                nextstate <= s3;
                out <= 1'd1;
            end else begin
                nextstate <= s4;
                out <= 1'd0;
            end
        end
    endcase
end

```

```

        end
    end

    s3: begin
        if (in) begin
            nextstate <= s1;
            out <= 1'd0;
        end else begin
            nextstate <= s4;
            out <= 1'd1;
        end
    end

    s4: begin
        if (in) begin
            nextstate <= s0;
            out <= 1'd1;
        end else begin
            nextstate <= s4;
            out <= 1'd0;
        end
    end

    default: begin
        nextstate <= nextstate;
        out <= out;
    end
endcase
end
endmodule

```


測試程式(testbench)
<pre> module stimulus; reg in, clk, reset; wire out; wire [2:0] currentstate, nextstate; count UUT (.clk(clk), .reset(reset), .in(in), .out(out), .currentstate(currentstate), </pre>

```


        .nextstate(nextstate)
    );
    initial begin
        clk = 1'b0;
        forever #5 clk = ~clk;
    end
    initial begin
        $monitor($time, " \t in = %b currentstate = %b nextstate = %b out = %b",
            in, currentstate, nextstate, out);
    end
    initial begin
        in = 1'b0; reset = 1'b0;
        #20 reset = 1'b1;
        #20 reset = 1'b0;
        #15 in = 1'b1;
        #30 in = 1'b0;
        #15 in = 1'b1;
        #15 in = 1'b0;
    end
    initial begin
        #150 $finish;
    end
endmodule

```

RTL schematic

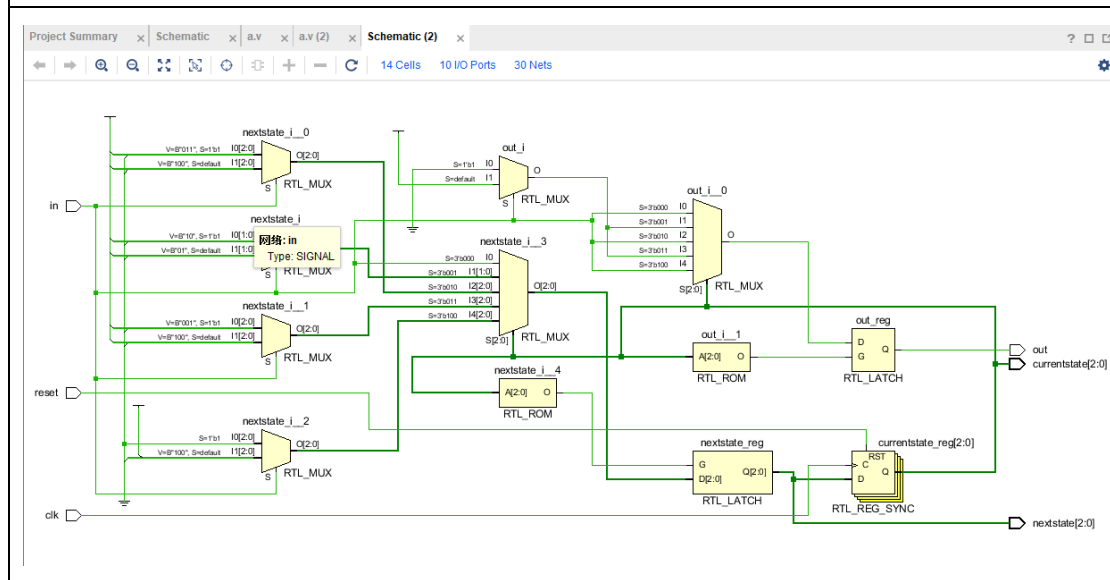

Technology Schematic

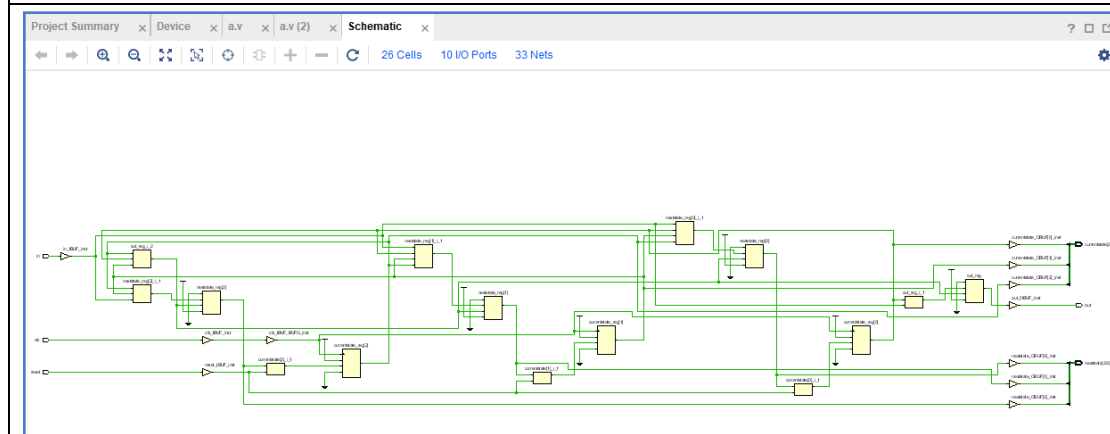

Behavioral Simulation Waveform(含 \$monitor)

